

# **Integrated Circuit Design**

## **Verilog Tutorial – part 1**

**Speaker : Yu-Cheng Li (d01943008@ntu.edu.tw)**

**Advisor : Yi-Chang Lu**

**Date : 2019.03.27**



# Outline

## ▪ Introduction

Part 1

## ▪ Verilog for RTL

- Module Description and Declaration
- Data Type and Operators
- Combinational Behavior
- Sequential Behavior

## - Finite State Machine

Part 2

## - Advanced Topics

## ▪ Design Example

## ▪ RTL Simulation Tool

## ▪ Synthesis Tool

Part 3

# Outline

## ▪ Introduction

## ▪ Verilog for RTL

- Module Description and Declaration
- Data Type and Operators
- Combinational Behavior
- Sequential Behavior
- Finite State Machine
- Advances Topics

## ▪ Design Example

## ▪ RTL Simulation Tool

## ▪ Synthesis


# Introduction

- **What is Verilog?**

- Hardware Description Language (HDL)
- Mostly use in digital design.

- **Why we need to learn Verilog?**

 - Millions or billions the number of transistors!
- We need EDA (Electronic design automation) tools.



# Verilog-Supported Levels of Abstraction

## ■ Behavior Level

- Modeling the circuit's behavior in high-level.

## ■ Register Transfer Level (RTL) We focus on RTL in this course.



- Describes the flow of data between registers and how a design process the data.

## ■ Gate Level

- Describes the logic gates and the interconnections.
  
## ■ Transistor Level

- Describes the transistors and the interconnections.




# Verilog-Supported Levels of Abstraction
 
## ▪ RTL

```
module mux2to1(in1, in2, sel, out)
  input in1, in2, sel;
  output out;


  always@(*) begin
    if(sel==0) out=in1;
    else out=in2;
  end
endmodule
```



 
## ▪ Gate Level

```
module mux2to1(in1, in2, sel, out)
  input in1, in2, sel;
  output out;
  wire inv_sel, a1_o, a2_o;

  and a1(a1_o, in1, iv_sel);
  not n1(inv_sel, sel);
  and a2(a2_o, in2, sel);
  or o1(out, a1_o, a2_o);
endmodule
```



# Cell-Based Design

 

# Summary

- Verilog is important for digital IC design
- Three level
  - RTL
  - Gate
  - Transistor



# Outline

- Introduction
- **Verilog for RTL**
  - **Module Description and Declaration**
  - **Data Type and Operators**
  - **Combinational Behavior**
  - **Sequential Behavior**
  - Finite State Machine
  - Advances Topics
- Design Example
- RTL Simulation Tool
- Synthesis

# Module Description and Declaration

```

4  module counter( clk, rst, down, num);
5  // --- Input/Output declaration
6  input      clk;
7  input      rst;
8  input      down;
9  output [3:0] num;

10
11 // --- MARCO declaration for FSM
12 parameter IDLE = 2'b00; // 2 bit binary 00
13 parameter DOWN = 2'd1;  // 2 bit decimal 1 equals to 00
14 parameter ZERO = 2'd2;
15
16 // --- Wire/ Reg declaration ---
17 reg [1:0] state, next_state;
18 reg [3:0] count;
19 reg [3:0] next_count;
20 reg [3:0] num, next_num;
21 wire [3:0] wire_next_num;
22

```

**module 宣告**

**MARCO**

**wire / reg 宣告**

```

56
57 // -----
58 // Sequential Part
59 // -----
60 always@(posedge clk or posedge rst)
61 begin
62     if(rst) begin
63         state <= IDLE;
64         count <= 4'd10;
65         num <= 4'd10;
66     end
67     else begin
68         state <= next_state;
69         count <= next_count;
70         num <= next_num;
71     end
72 end
73 endmodule
74

```

**Sequential Part**

**module 宣告**

```

22
23 // -----
24 // Combinational Part
25 // -----
26
27 // continuous assignment
28 assign wire_next_num = next_num;
29
30 // procedural assignment
31 always@(*) begin
32     case(state)
33     IDLE: begin
34         if (down==1'b1) next_state = DOWN;
35         else next_state = IDLE;
36         next_num = 4'd10;
37         next_count = (down ==1'b1) ? count-1'b1 :4'd10;
38     end
39     DOWN: begin
40         next_state = (count==4'd0) ? ZERO : DOWN;
41         next_count = (count==4'd0) ? 4'd0 : count-1'b1;
42         next_num = count;
43     end
44     ZERO: begin
45         next_state = IDLE;
46         next_count = 4'd10;
47         next_num = count;
48     end
49     default: begin
50         next_state = state;
51         next_count = count;
52         next_num = num;
53     end
54 endcase
55 end
56

```

**Combinational Part**

# Module Description and Declaration

- It's essential part and description of module interface.
- Basic format

```
module <module name> ( <port list> );  
    input  [vector length] <signal A> ;  
    input  [vector length] <signal B> ;  
    output [vector length] <signal C> ;  
    ...  
endmodule
```

- Example

```
module counter( clk, rst, down, num);  
    // --- Input/Output declaration  
    input      clk;  
    input      rst;  
    input      down;  
    output [3:0] num;  
endmodule
```

# Data Type and Operators

## ■ Number representation

`<number of bits>' <radix type> <value>`

- `4'd9` : means 4 bits in decimal 9 (`4'b1001` in binary)
- `10'b01`: means 10 bits in binary `00_0000_0001`
- `8'h10` : means 8 bits hexadecimal 10 (`8'b0001_0000` in binary)
- default value is decimal if there is no specific radix type
- Bad example : `4'd18`, `3'b6`, `6'hAB`....

## ■ Verilog support bitwise assignment

`<signal A> = f( < signal B> [N:M] ); // only used some bits`  
`<signal A> [ N:M] = <function value> // only assign some bits`

`A = 8'd12;`

`B = 8'h34;`

`A[7:4] = B[3:0];`

A: 

0	0	0	0	1	1	0	0
---	---	---	---	---	---	---	---

 $\Rightarrow$ 

0	1	0	0	1	1	0	0
---	---	---	---	---	---	---	---

B: 

0	0	1	1	0	1	0	0
---	---	---	---	---	---	---	---

# Data Type and Operators

## ■ Common used operators


Type	Operators	Examples	
Arithmetic	+, -, *, /, %	A = B+C;	1001 = 0111+0010
Bitwise	~, &,  , ^, ~^	A = B^C;	0101 = 0111^ 0010
Logical	!=, ==, &&,	A == B	0 = (0111 == 0101)
Relational	>, >=, <, <=	A>B	1 = (0111 > 0101)
Shift	>>, <<	A= B << 1;	1110 = 0111 << 1
Concatenation	{ }	A = {B, C}	0110 = {01, 10}

# Data Type and Operators

- Frequently used data type are “wire” and “reg”
- Basic format

wire [vector length] < variable name> [array size] ;

 reg [vector length] < variable name> [array size] ;



## ▪ Example

```
// --- Wire/ Reg declaration ---
reg  [1:0] state, next_state;
reg  [3:0] count;
reg  [3:0] next_count;
reg  [3:0] num,   next_num;
reg  [7:0] example_array [0:127]; //128 words, 8bit
wire [3:0] wire_next_num;
```

# Data Type and Operators

## ■ wire

- input / output port is set to wire as default.
- Value can **only** be changed by “assign”.

## ■ reg

- Value can **only** be changed by “always” block.

## ■ Example

```
// --- The use of wire and reg ----  
wire A,B,C;  
reg D;  
  
assign C = A & B;  
always@ (*)  
begin  
    D = A & B;  
end
```

# Data Type and Operators

## ▪ parameter

- “constant” in Verilog
- Basic format

```
parameter <variable name> = number;
```

## ▪ Example

```
// --- parameter ----  
parameter width = 3'd7;  
wire [width:0] w1;
```



# Combinational Behavior (1/4)

## ▪ Describing the combinational circuit has two style:

- Continuous assignment
- Procedural assignment

## ▪ Continuous assignment

```
assign <signal A> = <function value> ;
```

- Signal at left hand side(LHS) must be **wire** data type
- Signal function value at RHS can be wire or reg data type
- Ensure bit length is long enough

```
// --- Continuous assignment ----  
assign C = A & B;  
assign D = (A==B)?A:B;  
assign E = A + B;  
assign F = A << 2;
```

# Combinational Behavior (2/4)

## ■ Procedural assignment

```
always @(sensitivity list)
    <signal A> = <function value>;
```


- Signal at LHS must be **reg** datatype
- Signal at RHS can be reg or wire
- If there are 2 or more statements in always block, remember to add “begin” and “end”
- All signal in RHS must include in sensitivity list. (or use “\*”)

```
wire [3:0] inA, inB;
reg  [3:0] C, D;

always@(inA or inB or C)
begin
    C = inA+inB;
    D = C+1'b1;
end
```

```
wire [3:0] inA, inB;
reg  [3:0] C, D;

 always@(*)
begin
    C = inA+inB;
    D = C+1'b1;
end
```



# Combinational Behavior (3/4)

## ■ Conditional Statement

- For procedural assignment

```
case ( target )  
    condition1: statement1 ;  
    condition2: statement2 ;  
    ...  
    default:    statement N;  
endcase
```

```
if ( condition1 )  
    statement1 ;  
else if ( condition2 )  
    statement2 ;  
else  
    statement3 ;
```

```
case(en)  
    0: begin  
        out1 = inB;  
        out2 = 0;  
    end  
    1: begin  
        out1 = inA;  
        out2 = inA+inB;  
    end  
    default: begin  
        out1 = inB;  
        out2 = 0;  
    end  
endcase
```

※ Remember write all possible case or use default.

※ The incomplete case will cause a **Latch** after synthesis.

```
if(en==1'b1) begin  
    out1 = inA;  
    out2 = inA+inB;  
end  
else begin  
    out1 = inB;  
    out2 = 0;  
end
```

# Combinational Behavior (4/4)

## ▪ Conditional Statement


- For continuous assignment

```
assign signal A = ( condition ) ? ( True Signal ) : ( False Signal ) ;
```

```
assign out1 = (en==1'b1) ? inA : inB ;  
assign out2 = (en==1'b1) ? inA+inB : 0;
```

- You can't use if-else or case statement in continuous assignment statement.
 
```
if (en==1)  
    assign out1= inA;  
else  
    assign inB;
```



# Sequential Behavior (1/4)

## ▪ Describe the behavior of sequential circuit


```
always @ ( <sensitivity edge > <clock> [or <sensitivity edge> <reset >] )  
    if ( reset ) ... ;    // reset mode  
    else      ... ;    // normal mode
```

### Asynchronous reset

```
58 | [ ] |  
59 | [ ] |  
60 | [ ] |  
61 | [ ] |  
62 | [ ] |  
63 | [ ] |  
64 | [ ] |  
65 | [ ] |  
66 | [ ] |  
67 | [ ] |  
  
always @ (posedge clock or posedge reset) begin  
    if ( reset ) begin  
        state <= RED;  
        count <= 0;  
    end  
    else begin  
        state <= next_state;  
        count <= next_count;  
    end  
end
```


### Synchronous reset

```
58 | [ ] |  
59 | [ ] |  
60 | [ ] |  
61 | [ ] |  
62 | [ ] |  
63 | [ ] |  
64 | [ ] |  
65 | [ ] |  
66 | [ ] |  
67 | [ ] |  
  
always @ (posedge clock) begin  
    if ( reset ) begin  
        state <= RED;  
        count <= 0;  
    end  
    else begin  
        state <= next_state;  
        count <= next_count;  
    end  
end
```

 

# Sequential Behavior (2/4)
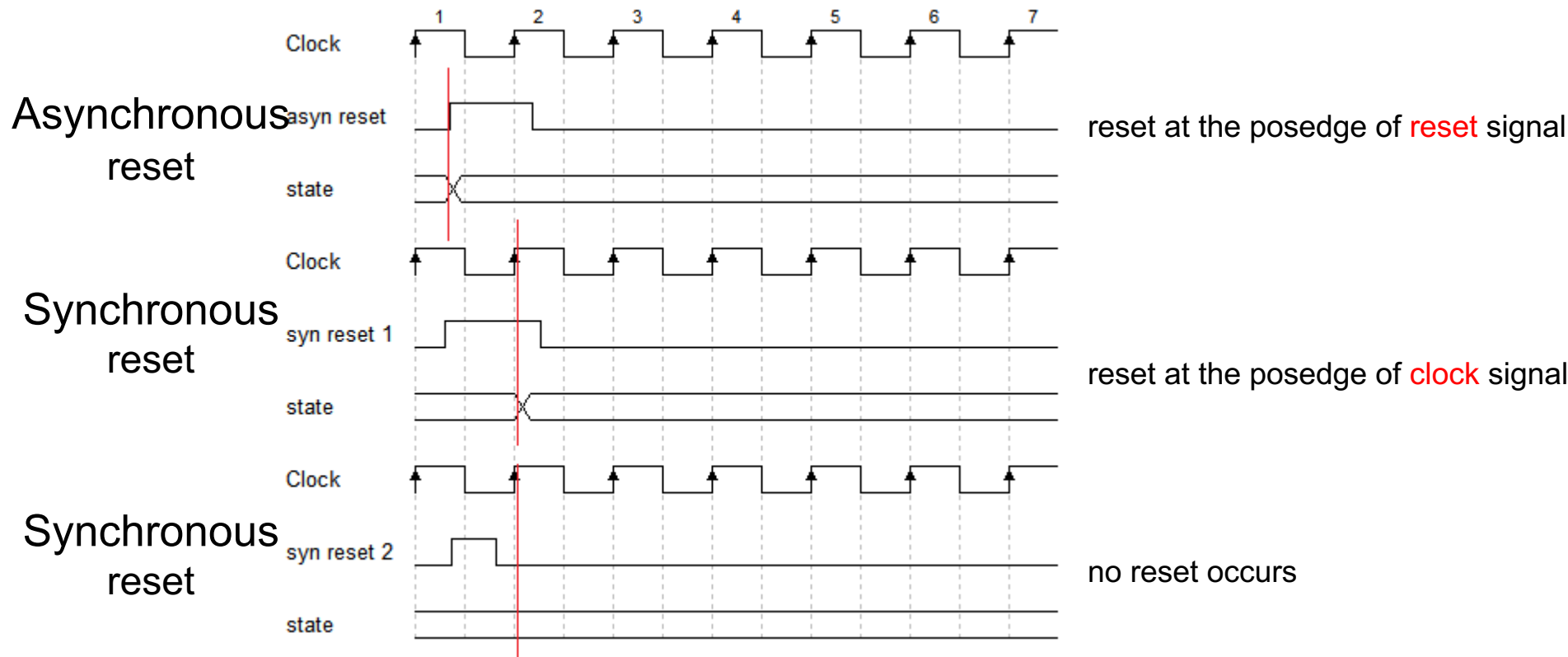
## ■ Difference between asynchronous reset and synchronous reset



※The circuit is synchronus to posedge clk and active high reset

# Sequential Behavior (3/4)

- The circuit must have a reset signal. Otherwise, the initial value of Flip-Flop will be unknown.
- Asynchronous or synchronous reset type depends on the circuit's spec.
- non-blocking assignment “<=” for sequential circuit.
- blocking assignment “=” for combinational circuit.

```
always @ (*) begin
    case( i_IDEX_AlucCtrl )
        4'b0000: AluResult = AluIn1 & AluIn2;
        4'b0001: AluResult = AluIn1 | AluIn2;
        4'b0101: AluResult = AluIn1 ^ AluIn2;
        4'b0110: AluResult = AluIn1 - AluIn2;
        4'b0111: AluResult = AluIn1 < AluIn2 ? 32'b1 : 32'b0;
        4'b1010: AluResult = AluIn2 << i_IDEX_Extend[10:6];
        4'b1101: AluResult = ~(AluIn1 | AluIn2);
        4'b1110: AluResult = AluIn2 >> i_IDEX_Extend[10:6];
        default: AluResult = AluIn1 + AluIn2;
    endcase
end
```

blocking assignment




```
always @ (posedge clock or posedge reset) begin
    if ( reset ) begin
        state <= RED;
        count <= 0;
    end
    else begin
        state <= next_state;
        count <= next_count;
    end
end
```


non-blocking assignment
 
# Sequential Behavior (4/4)

- Difference between non-blocking assignment and blocking assignment in synchronous block.


 
```
module block (q, d, clk);  
input d, clk;  
output q; reg q;  
reg tmp;  
always @(posedge clk)  
begin  
    tmp = d;  
    q = tmp;  
end  
endmodule
```



```
module noblock (q, d, clk);  
input d, clk;  
output q; reg q;  
reg tmp;  
always @(posedge clk)  
begin  
    tmp <= d;  
    q <= tmp;  
end  
endmodule
```